

5. Design a CMOS Level Shifter which can shift level VDDL of 0.5 V to $VDDH = 1V$