

3. Design Schematic and simulate a Master-Slave FF.

**Assignment-2 (10 Marks): Last Date for Submission is 30<sup>th</sup> April 2023**