

5. Design a CMOS Level Shifter which can shift level VDDL of 0.5 V to  $VDDH = 1V$