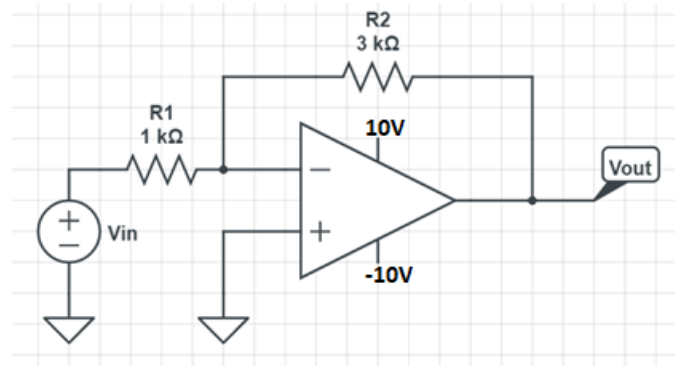


2) For the circuit shown, answer the following questions:



- What is the type of op-amp configuration in the above circuit? (2 pts)
- What are the minimum and maximum output voltage possible as per this circuit assuming an ideal op-amp? (2 pts)
- What is the gain in the above circuit? (2 pts)
- What are the minimum and maximum input voltage values that can be provided to the above circuit without saturating the output? (2 pts)
- Sketch the output waveform for the given input waveform. Mark the amplitude values. (2 pts)

