

4. Design a CMOS Schmitt trigger circuit with hysteresis width 500 mV approximately and simulate.