## \_\_\_\_\_\_ 2. Design Schematic and simulate a D latch using transmission gates.