

1. Design Schematic and simulate a SR-Latch.